

CamJam EduKit Sensors Worksheet Four

Project Light Sensor

Description In this project, you will learn how to detect how bright it is in your room.

Equipment Required

- Your Raspberry Pi
- 400 Point Breadboard
- LDR - Light Dependent Resistor
- 3 x Male-Male jumper wires
- 3 x Male-Female jumper wires
- 1uf Capacitor

The Parts

Two parts you will use may not be familiar to you.

Light Dependent Resistor



A Light Dependent Resistor – or LDR – is a resistor whose resistance changes depending on how much light is falling on its surface.

It will not accurately measure the light, but just measures the change in light falling on the sensor. For example, it could be used to see whether it is light or dark in a room.

Capacitor



A capacitor is an electronic device that stores electric energy. It is similar to a battery, but is smaller, lightweight and charges up much quicker.

Capacitors are usually made with two metal plates that are on top of each other and near each other, but that do not actually touch. When powered, they allow energy to be stored inside an electrical field. Because the plates need a lot of area to store even a small amount of charge, the plates are usually rolled up into some other shape, such as a cylinder.


The capacity of a capacitor is measured in Farads. Because a Farad is a large number, capacitors are often labelled in micro (μ) Farads, or μ F.

As with batteries, there is a negative and a positive leg. The negative leg is the one that is usually marked – in this case with a white bar.

In this circuit it is being used as a way to convert an analogue signal (the resistance of the LDR) by timing how long it takes to charge the capacitor, which will depend on how much energy is supplied to the capacitor, and in turn that is limited by the resistance the LDR gives to the flow of energy in the circuit.

Building the Circuit

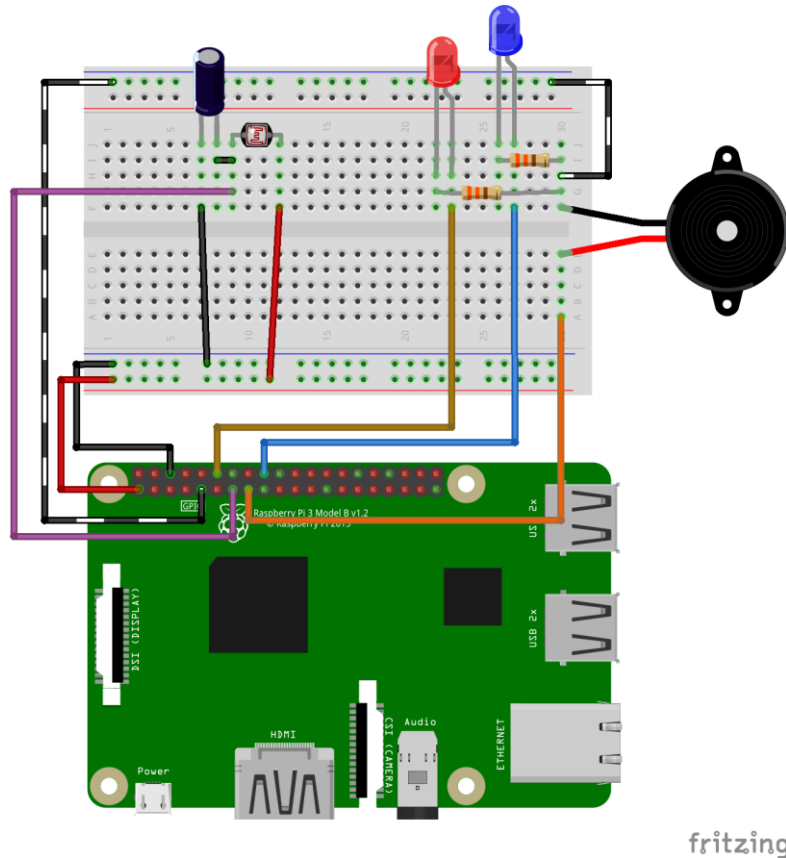Turn the Raspberry Pi off before building this circuit.



Build the circuit as shown in the diagram on the left, leaving the buzzer and LED circuit in place.

The left leg of the capacitor in the diagram is the negative leg, marked by the white bar. The negative leg of the capacitor is connected to 'ground' on the Pi, and the positive leg is connected to the 3.3v of the Pi via the LDR.

The resistance of the LDR will affect how quickly the capacitor will charge up, which is read by Pin 27 of the Raspberry Pi. The higher the resistance, the longer it takes to charge.

Note the wire between the positive leg of the capacitor and the LDR. This is a jumper with a pin at each end.

Code

Open the IDLE3 editor and type in the following code:

```
# CamJam Edukit 2 - Sensors
# Worksheet 4 - Light

# Import Libraries
import time
import RPi.GPIO as GPIO

# Set the GPIO Mode
GPIO.setmode(GPIO.BCM)
GPIO.setwarnings(False)

# A variable with the LDR reading pin number
PinLDR = 27

def ReadLDR():
    LDRCount = 0 # Sets the count to 0
    GPIO.setup(PinLDR, GPIO.OUT)
    GPIO.output(PinLDR, GPIO.LOW)
    time.sleep(0.1) # Drains all charge from the capacitor
```

```
GPIO.setup(PinLDR, GPIO.IN) # Sets the pin to be input
# While the input pin reads 'off' or Low, count
while (GPIO.input(PinLDR) == GPIO.LOW):
    LDRCount += 1 # Add one to the counter
return LDRCount

while True:
    print(ReadLDR())
    time.sleep(1) # Wait for a second
```

Save the file as 4-LDR.py in the EduKitSensors directory.

Running the Code

Select the Run Module menu option, under the Run menu item. Alternatively, you can just press the F5 key. Change the light intensity by covering up the LDR, or shining a light at the LDR. Watch the readings change.

How the Circuit Works

So, how does the circuit measure how much light is falling on the LDR?

When the function ReadLDR is called, the measurement pin (PinLDR) is first set to be an output pin and is set to 'low', or 0 volts, for a short time. This will empty the capacitor of charge.

The measurement pin will then be set as an input pin, which will then detect the voltage across the capacitor. Because the Raspberry Pi GPIO input is digital only, it only knows when the input is either 'off' (0v) or on (3.3v). The Pi actually considers any voltage on an input pin that is between 0 and about 1.4v to be 'off' (or 0), and anything between 1.4v and 3.3v to be 'on'.

As the capacitor charges up, the Pi is able to time how long it takes for the input pin to change from 'off' to 'on' by using a simple counter (LDRCount). LDRCount represents how much light is on the resistor. The brighter the light, the lower the resistance the LDR provides, and therefore the quicker the capacitor charges and the lower the value of LDRCount.

LDRs are not accurate pieces of electronics. Each one will differ. Therefore, they cannot be used to accurately measure how bright the light falling on them is. In addition, if other programs are running on the Pi, the counter loop may run a little slower.

Challenge

Extend the code above to turn on the LEDs under chosen conditions. As mentioned above, each LDR measures light brightness differently, therefore you are free to choose at what light level you turn the LEDs on and off.

By taking some code from Worksheet 2 (LEDs and Buzzer), add 'if' statements to:

- Turn on the red LED when the light falling on the LDR is bright, and turn it off when it is not as bright.
- Turn on the blue LED when it is dull, and off when it gets brighter.
- If the light gets really bright, sound the buzzer.